NTUEE DCLAB

LAB 1: 亂數點名器

Graduate Institute of Electronics Engineering
National Taiwan University

- Introduction
 - Lab requirements
- Implementation
 - Finite state machine (FSM) and count down control
 - Generating random numbers
 - Reset signal
- Code template
- Simulation and debug
- Report regulations

Introduction



https://www.youtube.com/watch?v=FwTzURTGyvc

Lab Requirements

- 按下key1可以reset
- 按下key0可開始點名器運作
 - 隨機產生0~15的亂數
 - 以七段顯示器顯示
 - 數字跳動頻率逐漸變慢
 - 最後停在一個數字上



- Bonus (demo時與report中皆應清楚詳細說明)
 - 跳動中途擷取亂數
 - 記憶前次亂數結果
 - 其他能想到的創意


- Introduction
 - Lab requirements
- Implementation
 - Finite state machine (FSM) and count down control
 - Generating random numbers
 - Reset signal
- Code template
- Simulation and debug
- Report regulations

Finite State Machine (FSM) Design

• 簡單範例

- IDLE: 等待key0被按下

- RUN:產生亂數並變動輸出切換頻率

 


Think

- 如何變動輸出切換頻率?
 - 用 counter 計算每經過幾個 cycle 要輸出 (內建的clock是50MHz)
 - 用更多 state 來切換停留在一數字上的時間
 - 等等

Random Number Generation

 - 電路上通常都是產生 pseudo-random number
 - Linear feedback shift register (LFSR)



Linear congruential generator

$$X_{n+1} = aX_n + b \pmod{M}$$

- Think
 - 如何在每次按下 key0 後產生不同的亂數數列?
 - Seed 如何產生與設定?

Reset Signal


- 按下key1會產生global reset signal
 - 將所有register設定為初始值
- 寫在sequential block裡面

```
always_ff @(posedge i_clk or posedge i_rst) begin
        if (i rst) begin
                state r <= IDLE;</pre>
                counter r <= 9'd0;
                o_ans_r <= 258'd0;
                o_finish_r <= 1'b0;
        end
        else begin
                state_r <= state_w;</pre>
                counter_r <= counter_w;</pre>
                o ans r <= o ans w;
                o finish r <= o finish w;
        end
```

- Introduction
 - Lab requirements
- Implementation
 - Finite state machine (FSM) and count down control
 - Generating random numbers
 - Reset signal
- Code template
- Simulation and debug
- Report regulations

Code Template

 - DE2_115.qsf
 - Map top-level I/O to FPGA physical I/O
- DE2_115.sdc
 - Timing constraints
- DE2_115.sv
 - Top module mapped to FPGA
- Debounce.sv
 - Stabilize key press glitch
 - Provide 1-clock-pulse keydown/keyup signal
- SevenHexDecoder.sv



Code TODO

Add your code to Top.sv

```
– always_comb
```

– always_ff

```
module Top (
             input
                           i_clk,
 3
             input
                           i_rst_n,
             input
4
                           i_start,
             output [3:0] o_random_out
5
    );
    // please check out the working example in lab1 README first
8
9
    endmodule
10
```


- Introduction
 - Lab requirements
- Implementation
 - Finite state machine (FSM) and count down control
 - Generating random numbers
 - Reset signal
- Code template
- Simulation and debug
- Report regulations

Run Testbench on Server


- Login to server
- Keep the provided directory structure
- Source the EDA tools (for neverilog, Verdi)
- > cd lab1/sim/
- > ncverilog tb_Top.sv ./../src/Top.sv +access+rw
- > nWave &

Debug with Waveform

 Type "nWave &" and open the waveform file



Choose the signals you wish to observe

 

- Introduction
 - Lab requirements
- Implementation
 - Finite state machine (FSM) and count down control
 - Generating random numbers
 - Reset signal
- Code template
- Simulation and debug
- Report regulations

Report Regulations

- 內容應包含
 - 層級架構
 - Block Diagram (必須包含Data Path, control signal可有可無)
 - FSM or Scheduling
 - Fitter Summary截圖
 - Timing Analyzer截圖
 - 遇到的問題與解決辦法
- 一組交一份,以pdf檔繳交
- 命名方式:teamXX_lab1_report.pdf
 - Ex: team01_lab1_report.pdf
- 繳交期限:demo當天午夜
 - 遲交每三天*0.7

Submission Rules

• 繳交檔案架構

```
team01_lab1
|-team01_lab1_report.pdf
|-src
|-<all of your verilog code>.v
```

- 將 teamXX_labX 資料夾包成一個 zip 後,上傳到實驗室 NAS 各組的 submission 資料夾
- src 資料夾內的 Verilog 可自行命名,只要在 report 中有 說明層級架構即可
- 繳交期限: demo 日當天 23:59 前
- 若未遵守繳交格式會酌情扣分

Questions?

NTUEE DCLAB 18